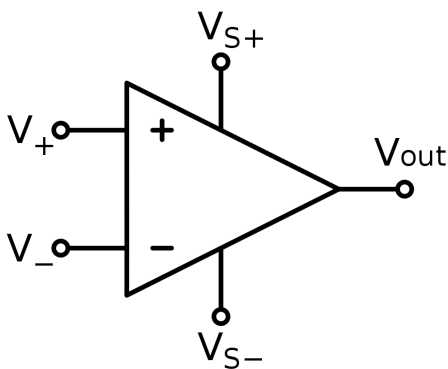


# Lecture-3

- Lecture-3
  - Operational Amplifier
    - Open-loop Amplifier
    - Closed-loop Amplifier
  - Inverting Amplifier
  - Noninverting Amplifier
  - Summing Amplifier
  - Difference Amplifier
  - Reference

## Operational Amplifier




the amplifier's differential inputs consist of a non-inverting input(+) with voltage  $V_+$  and an inverting input(-) with voltage  $V_-$

ideally the op amp amplifies only the difference in voltage between the two and the output voltage of the op amp  $V_{out}$  is given by the equation

$$V_{out} = A_{OL}(V_+ - V_-)$$

where  $A_{OL}$  is the open-loop gain of the amplifier <sup>1</sup>


## Open-loop Amplifier

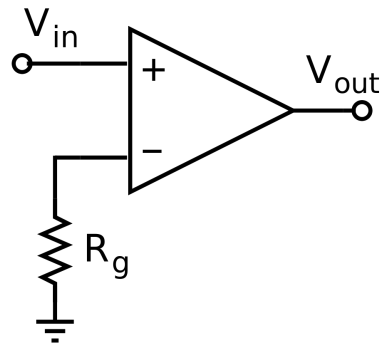

Since the magnitude of  $A_{OL}$  is typically very large, the op amp without negative feedback will work as a comparator. <sup>2</sup>


$$V_{out} = \begin{cases} +\infty & V_{in} > 0 \\ -\infty & V_{in} < 0 \end{cases}$$

## Closed-loop Amplifier

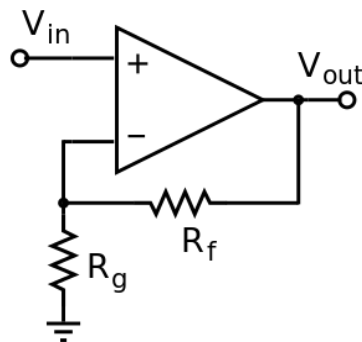

- $V_+ = V_-$ : when an op amp operates in linear mode, the **difference in voltage** between the non-inverting (+) pin and the inverting (-) pin is **negligibly small**
- $I_{in} = 0$ : the **input impedance** between (+) and (-) pins is **much larger** than other resistances in the circuit <sup>3</sup>


## Inverting Amplifier

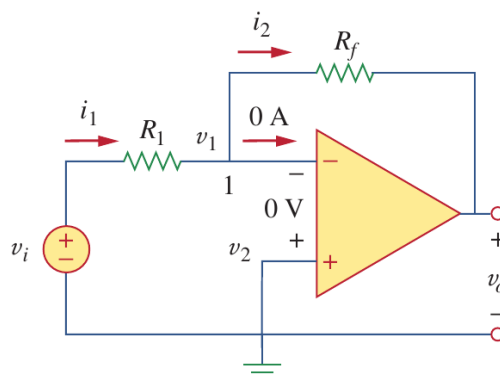

$$\frac{v_i - v_1}{R_1} = \frac{v_1 - v_0}{R_f}$$


$$v_0 = -\frac{R_f}{R_1}v_i$$

## Noninverting Amplifier

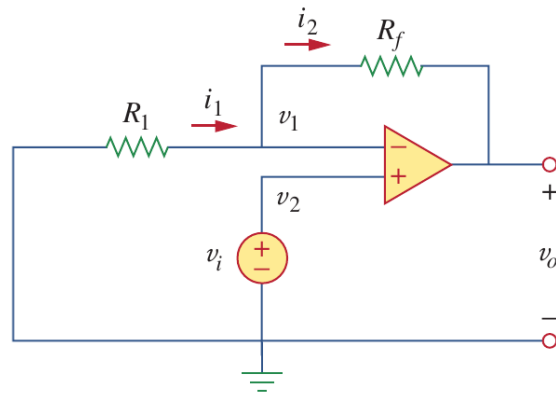


$$\frac{0 - v_i}{R_1} = \frac{v_i - v_0}{R_f}$$
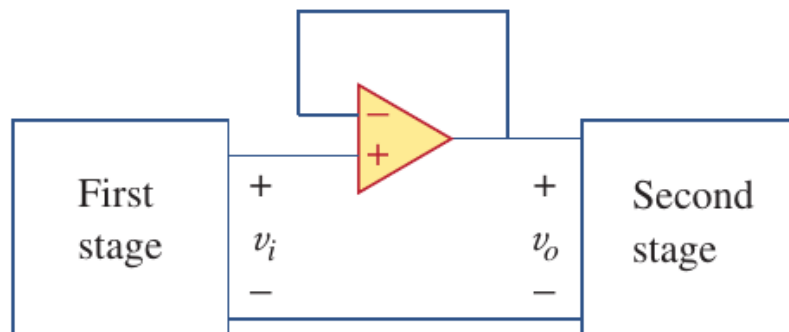
$$v_0 = \left(1 + \frac{R_f}{R_1}\right)v_i$$



$$v_0 = v_i$$


## Summing Amplifier

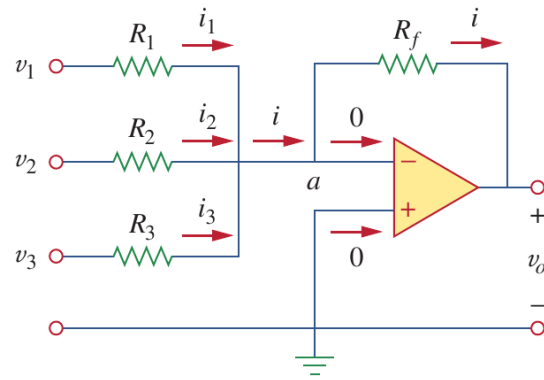

$$\frac{0 - v_0}{R_f} = \frac{v_1 - 0}{R_1} + \frac{v_2 - 0}{R_2} + \frac{v_3 - 0}{R_3}$$

$$v_0 = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$$

## Difference Amplifier

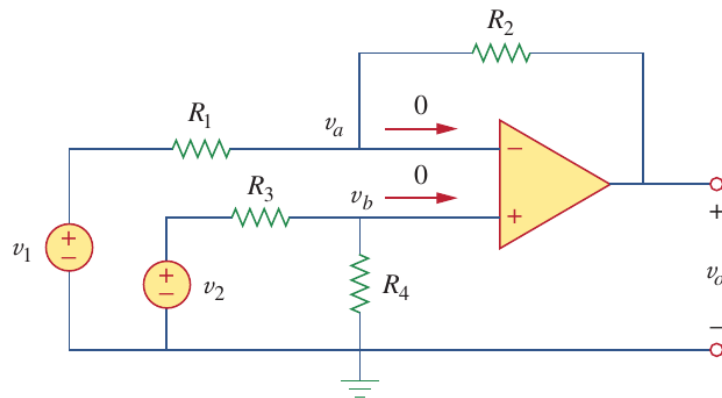

$$\begin{cases} \frac{v_1 - v_a}{R_1} = \frac{v_a - v_0}{R_2} \\ v_a = v_b = \frac{R_4}{R_3 + R_4} v_2 \end{cases} \implies v_0 = \frac{R_2(1 + R_1/R_2)}{R_1(1 + R_3/R_4)} v_2 - \frac{R_2}{R_1} v_1$$

## Reference

- [1] [Operational amplifier - 1 Operation - Wikipedia](#)
- [2] [Operational amplifier - 1.1 Open-loop amplifier - Wikipedia](#)
- [2] [Operational amplifier - 1.2 Closed-loop amplifier - Wikipedia](#)